

微算機系統

小組專案報告

實驗七：

八位元除法器

組別： 20

班級、姓名與學號：

醫工三 葉芸茜 B812110004

醫工三 湯青秀 B812110011

日期：112年12月15日

一、實驗內容：

1. 請設計出一個可進行觸發的除法運算的電路系統
2. 必須透過移位暫存器配合實驗六運算方式，實現電路架構圖完成本次實驗
3. 測試時，以按鈕改變clock觸發事件進行運算並顯示結果
4. 除數與被除數輸入範圍為1-255，需顯示除法運算後的商與餘數結果
5. 可使用GENERIC以及PROCESS內之FOR LOOP
6. 需使用實驗五的多用途移位暫存器
7. 正確顯示“商”(Quotient)跟“餘”(Remainder)之結果於LED上。並在完成計算時(狀態機到達S4)，以16進制正確顯示“商”(Quotient)跟“餘”(Remainder)之結果於七段顯示器上


Variable	Pin Location	Signal Name
clk	PIN_M23	KEY[0]
output[0]	PIN_F19	LED[1]
output[1]	PIN_E19	LED[2]
output[2]	PIN_F21	LED[3]
Divisor(0)	PIN_AB28	SW[0]
Divisor(1)	PIN_AC28	SW[1]
Divisor(2)	PIN_AC27	SW[2]
Divisor(3)	PIN_AD27	SW[3]
Divisor(4)	PIN_AB27	SW[4]
Divisor(5)	PIN_AC26	SW[5]
Divisor(6)	PIN_AD26	SW[6]
Divisor(7)	PIN_AB26	SW[7]
Dividend(0)	PIN_AC25	SW[8]
Dividend(1)	PIN_AB25	SW[9]
Dividend(2)	PIN_AC24	SW[10]

Dividend(3)	PIN_AB24	SW[11]
Dividend(4)	PIN_AB23	SW[12]
Dividend(5)	PIN_AA24	SW[13]
Dividend(6)	PIN_AA23	SW[14]
Dividend(7)	PIN_AA22	SW[15]
clear	PIN_Y24	SW[16]
a0	PIN_G18	HEX0[0]
b0	PIN_F22	HEX0[1]
c0	PIN_E17	HEX0[2]
d0	PIN_L26	HEX0[3]
e0	PIN_L25	HEX0[4]
f0	PIN_J22	HEX0[5]
g0	PIN_H22	HEX0[6]
a1	PIN_M24	HEX1[0]
b1	PIN_Y22	HEX1[1]
c1	PIN_W21	HEX1[2]
d1	PIN_W22	HEX1[3]
e1	PIN_W25	HEX1[4]
f1	PIN_U23	HEX1[5]
g1	PIN_U24	HEX1[6]
a2	PIN_AA25	HEX2[0]
b2	PIN_AA26	HEX2[1]
c2	PIN_Y25	HEX2[2]
d2	PIN_W26	HEX2[3]
e2	PIN_Y26	HEX2[4]
f2	PIN_W27	HEX2[5]

g2	PIN_W28	HEX2[6]
a3	PIN_V21	HEX3[0]
b3	PIN_U21	HEX3[1]
c3	PIN_AB20	HEX3[2]
d3	PIN_AA21	HEX3[3]
e3	PIN_AD24	HEX3[4]
f3	PIN_AF23	HEX3[5]
g3	PIN_Y19	HEX3[6]
Quotient(0)	PIN_G19	LED[0]
Quotient(1)	PIN_F19	LED[1]
Quotient(2)	PIN_E19	LED[2]
Quotient(3)	PIN_F21	LED[3]
Quotient(4)	PIN_F18	LED[4]
Quotient(5)	PIN_E18	LED[5]
Quotient(6)	PIN_J19	LED[6]
Quotient(7)	PIN_H19	LED[7]
Remainder(0)	PIN_J17	LED[8]
Remainder(1)	PIN_G17	LED[9]
Remainder(2)	PIN_J15	LED[10]
Remainder(3)	PIN_H16	LED[11]
Remainder(4)	PIN_J16	LED[12]
Remainder(5)	PIN_H17	LED[13]
Remainder(6)	PIN_F15	LED[14]
Remainder(7)	PIN_G15	LED[15]

二、實驗過程及結果：

(一) 預期實驗結果的流程示意圖

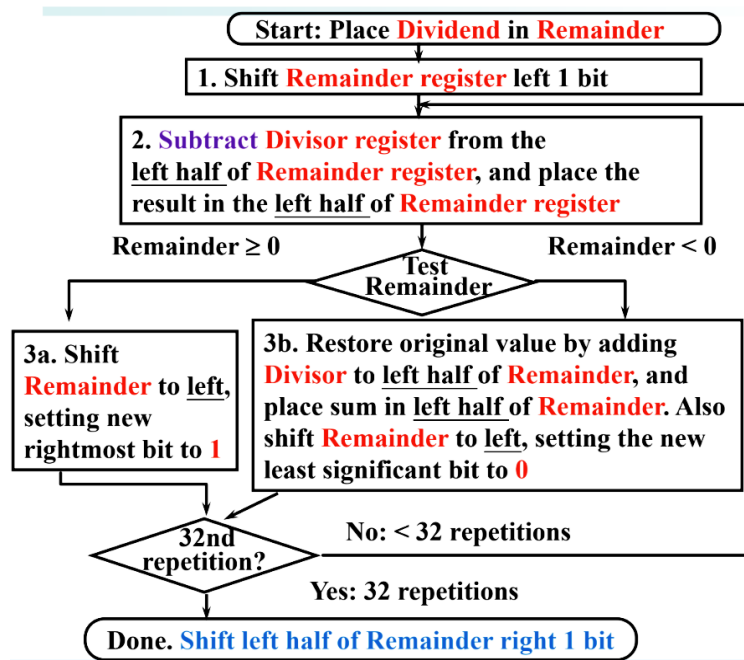

(二) 設計電路示意圖

Main →

process 1 = FSM.

case 1: $\text{temp-s} \leftarrow (\text{左半 remainder} - \text{除數}) (\text{右半 remainder})$

case 2: $\text{temp-p} \leftarrow (\text{左半 remainder} + \text{除數}) (\text{右半 remainder})$

process 2: output select


process 3: count 次數 → 數到 8 次時 run = 0

select W → "01" 時, 如果 temp-s 最高位為 1 → W=0.

"011", "010" 時, 如果還沒到 8 次 → W=0.


七段顯示器

process 1: FSM

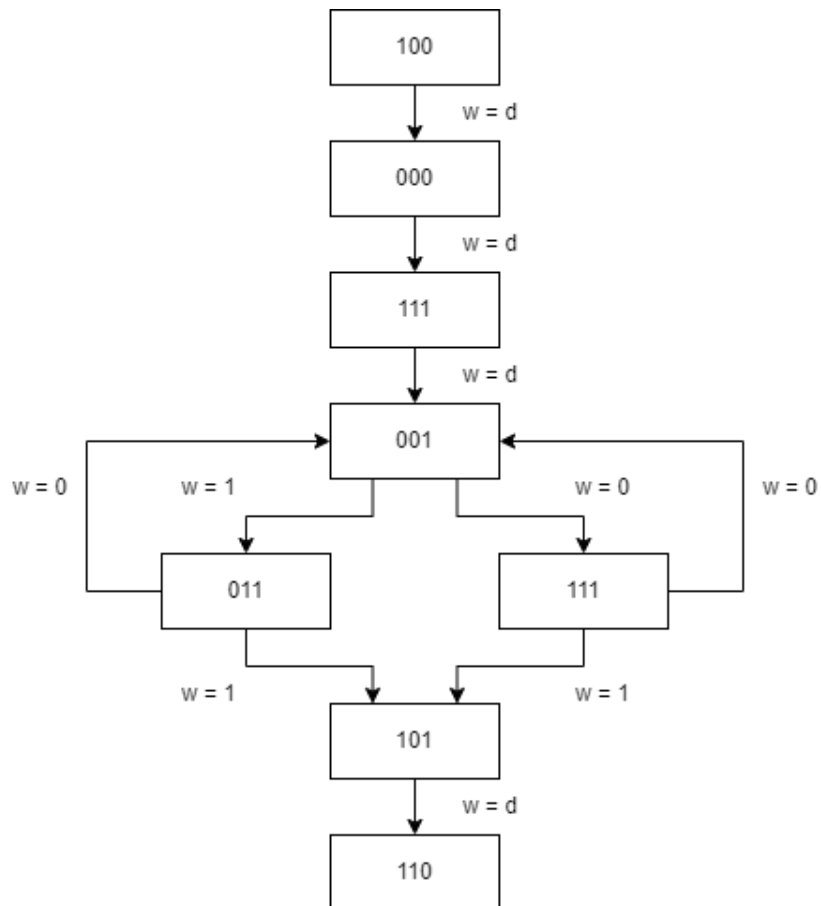



<https://drive.google.com/file/d/1SFREBBdMMrIMH7U2qnHV2TXyJ2KqXx-2/view?usp=sharing>


(三) 設計出的電路

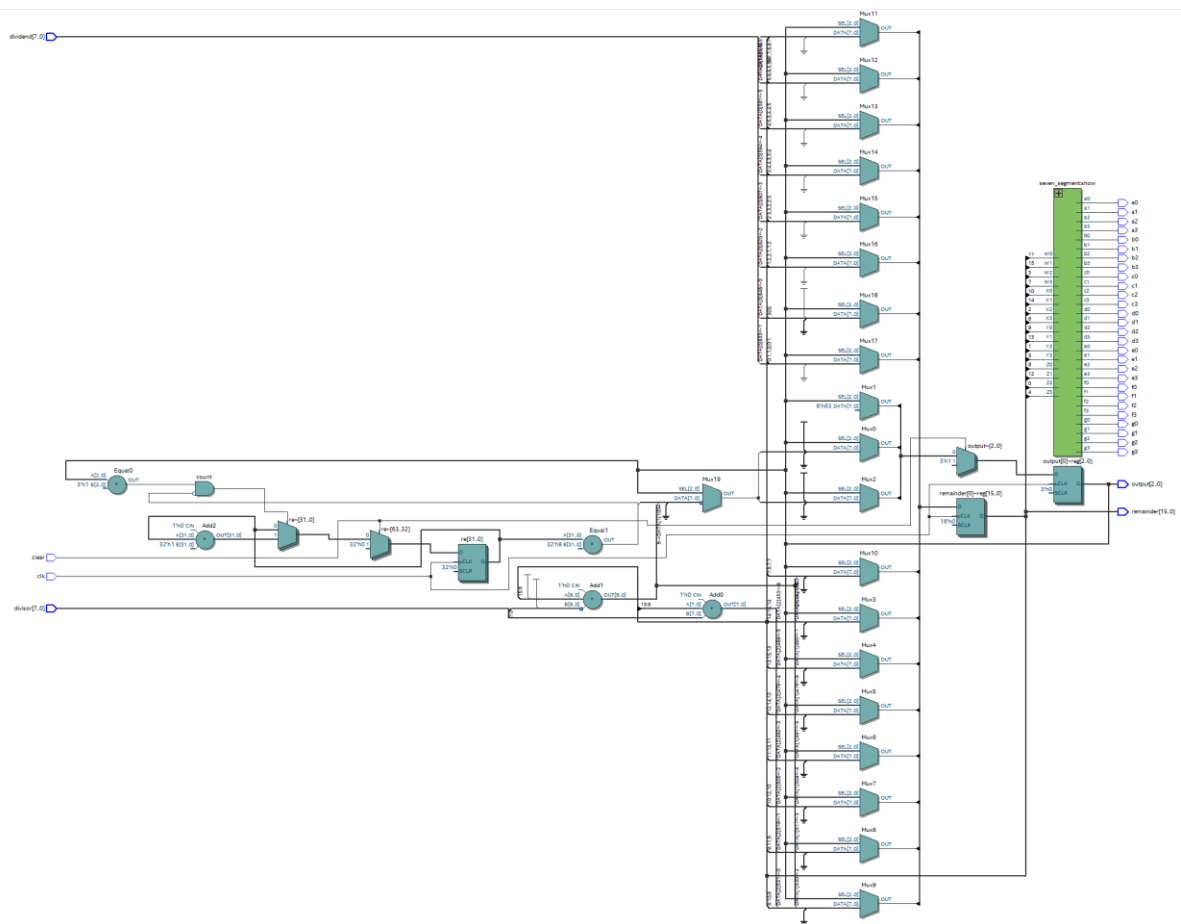


(四) 實驗過程

(1) 撰寫程式碼

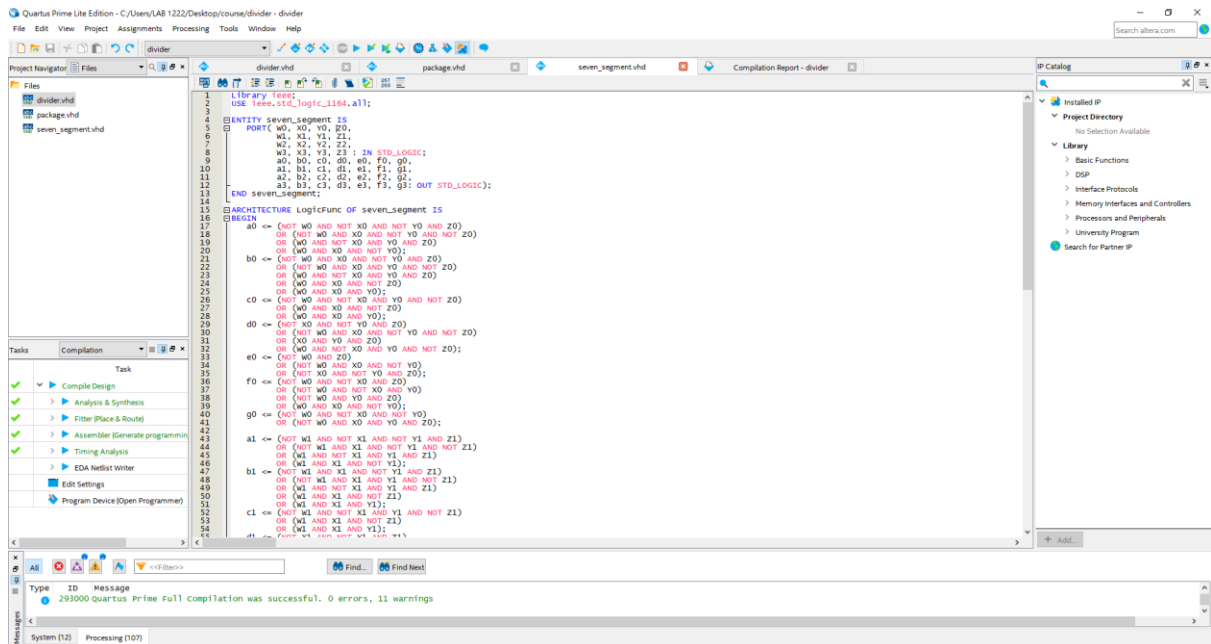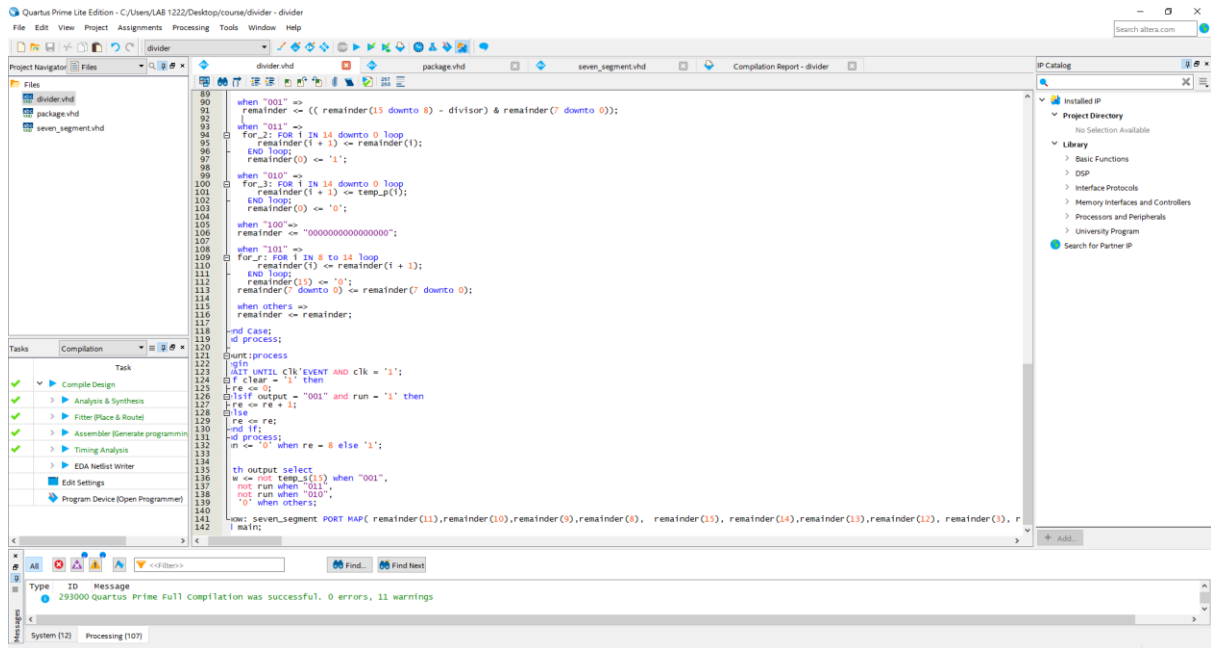

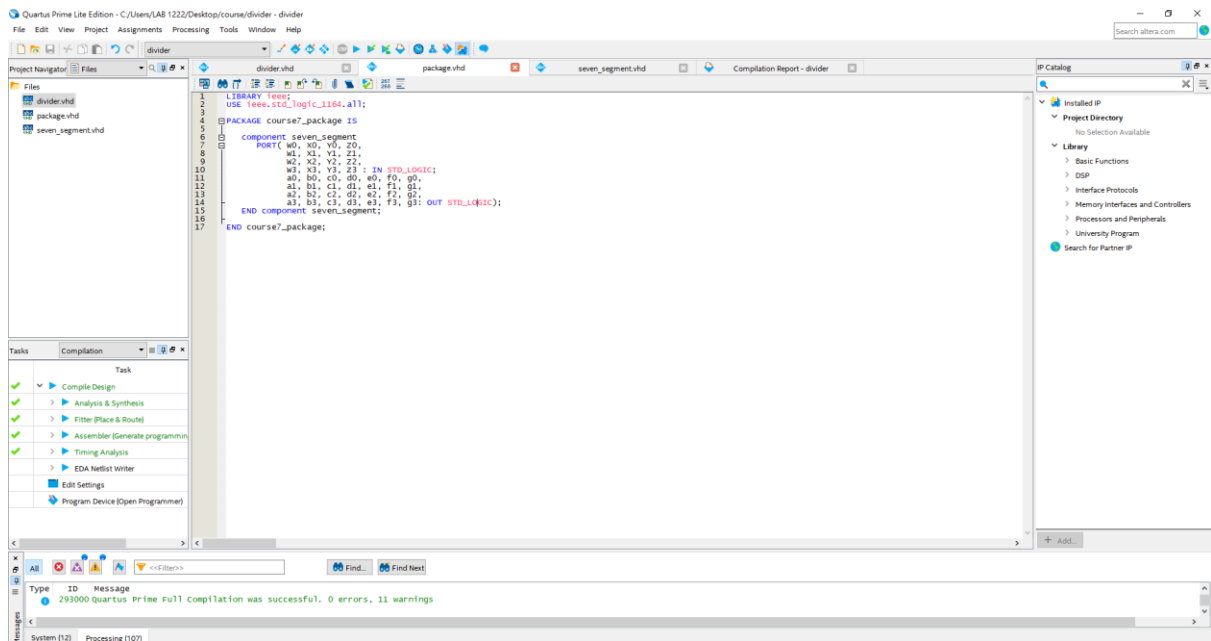

(2) 編譯成功

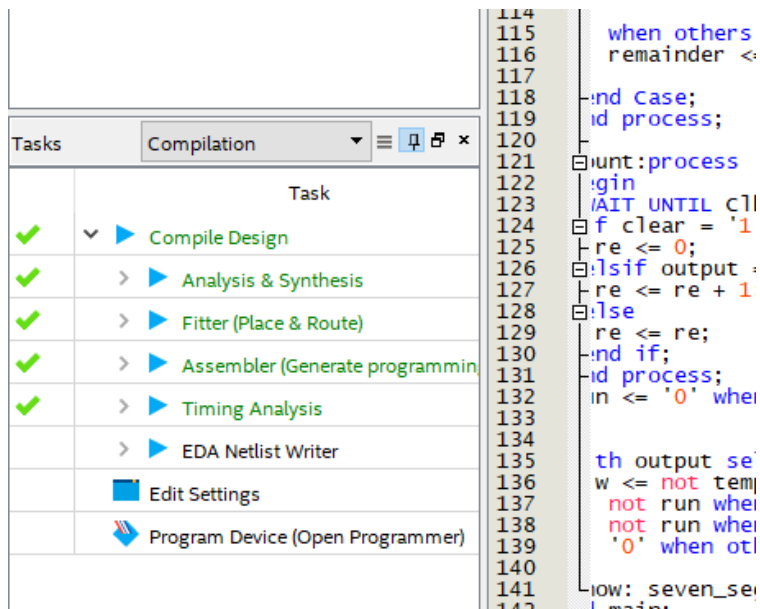

(3) 接腳位

Pin Planner - C:\Users\LAB 1222\Desktop\course\divider - divider

File Edit View Processing Tools Window Help

Report not available

Groups Report

Tasks

Early Pin Planning

Early Pin Planning

Pin Legend

Symbol Pin Type

- User I/O
- User assigned I.
- Filter assigned I.
- Unbonded pad
- Reserved pin
- Other configura...
- DEV_OE
- DEV_CLK

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	Strict Preservation
a0	Output	PN_C18	7	B7_N2	PN_C16	2.5 V (default)		8mA (default)	2 (default)		
a1	Output	PN_m24	6	B6_N2	PN_A10	2.5 V (default)		8mA (default)	2 (default)		
a2	Output	PN_ab25	5	B5_N1	PN_D8	2.5 V (default)		8mA (default)	2 (default)		
a3	Output	PN_v21	5	B5_N1	PN_A6	2.5 V (default)		8mA (default)	2 (default)		
b0	Output	PN_y22	7	B7_N0	PN_E15	2.5 V (default)		8mA (default)	2 (default)		
b1	Output	PN_y22	5	B5_N0	PN_D10	2.5 V (default)		8mA (default)	2 (default)		
b2	Output	PN_ab26	5	B5_N1	PN_G8	2.5 V (default)		8mA (default)	2 (default)		
b3	Output	PN_u21	5	B5_N0	PN_D11	2.5 V (default)		8mA (default)	2 (default)		
c0	Output	PN_w17	7	B7_N2	PN_C15	2.5 V (default)		8mA (default)	2 (default)		
c1	Output	PN_w21	5	B5_N1	PN_B10	2.5 V (default)		8mA (default)	2 (default)		
c2	Output	PN_y25	5	B5_N1	PN_E7	2.5 V (default)		8mA (default)	2 (default)		
c3	Output	PN_ab20	4	B4_N0	PN_G10	2.5 V (default)		8mA (default)	2 (default)		
clear	Input	PN_y24	5	B5_N2	PN_G13	2.5 V (default)		8mA (default)	2 (default)		
clk	Input	PN_m23	6	B6_N2	PN_J1	2.5 V (default)		8mA (default)	2 (default)		
d0	Output	PN_l26	6	B6_N1	PN_F15	2.5 V (default)		8mA (default)	2 (default)		
d1	Output	PN_w22	5	B5_N0	PN_H13	2.5 V (default)		8mA (default)	2 (default)		
d2	Output	PN_w26	5	B5_N1	PN_C8	2.5 V (default)		8mA (default)	2 (default)		
d3	Output	PN_aa21	4	B4_N0	PN_H12	2.5 V (default)		8mA (default)	2 (default)		
divider[7]	Input	PN_ab22	5	B5_N2	PN_J10	2.5 V (default)		8mA (default)	2 (default)		
divider[6]	Input	PN_ab23	5	B5_N2	PN_J12	2.5 V (default)		8mA (default)	2 (default)		
divider[5]	Input	PN_ab24	5	B5_N2	PN_A7	2.5 V (default)		8mA (default)	2 (default)		
divider[4]	Input	PN_ab23	5	B5_N2	PN_H10	2.5 V (default)		8mA (default)	2 (default)		
divider[3]	Input	PN_ab24	5	B5_N2	PN_E11	2.5 V (default)		8mA (default)	2 (default)		
divider[2]	Input	PN_ab24	5	B5_N2	PN_E7	2.5 V (default)		8mA (default)	2 (default)		
divider[1]	Input	PN_ab25	5	B5_N1	PN_J27	2.5 V (default)		8mA (default)	2 (default)		
divider[0]	Input	PN_ac25	5	B5_N2	PN_J28	2.5 V (default)		8mA (default)	2 (default)		
divisor[7]	Input	PN_ab26	5	B5_N1	PN_F14	2.5 V (default)		8mA (default)	2 (default)		
divisor[6]	Input	PN_ab26	5	B5_N2	PN_H14	2.5 V (default)		8mA (default)	2 (default)		
divisor[5]	Input	PN_ac26	5	B5_N2	PN_A17	2.5 V (default)		8mA (default)	2 (default)		
divisor[4]	Input	PN_ab27	5	B5_N1	PN_J14	2.5 V (default)		8mA (default)	2 (default)		
divisor[3]	Input	PN_ab27	5	B5_N2	PN_C13	2.5 V (default)		8mA (default)	2 (default)		
divisor[2]	Input	PN_ac27	5	B5_N2	PN_D14	2.5 V (default)		8mA (default)	2 (default)		
divisor[1]	Input	PN_ac28	5	B5_N2	PN_D13	2.5 V (default)		8mA (default)	2 (default)		
divisor[0]	Input	PN_ab28	5	B5_N1	PN_A12	2.5 V (default)		8mA (default)	2 (default)		

Pin Planner - C:\Users\LAB 1222\Desktop\course\divider - divider

File Edit View Processing Tools Window Help

Report not available

Groups Report

Tasks

Early Pin Planning

Early Pin Planning


Pin Legend

Symbol Pin Type


- User I/O
- User assigned I.
- Filter assigned I.
- Unbonded pad
- Reserved pin
- Other configura...
- DEV_OE
- DEV_CLK

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	Strict Preservation
divisor[1]	Input	PN_ac28	5	B5_N2	PN_D13	2.5 V (default)		8mA (default)	2 (default)		
divisor[0]	Input	PN_ab28	5	B5_N1	PN_A12	2.5 V (default)		8mA (default)	2 (default)		
e0	Output	PN_l25	6	B6_N1	PN_H15	2.5 V (default)		8mA (default)	2 (default)		
e1	Output	PN_w25	5	B5_N1	PN_J12	2.5 V (default)		8mA (default)	2 (default)		
e2	Output	PN_y26	5	B5_N1	PN_D7	2.5 V (default)		8mA (default)	2 (default)		
e3	Output	PN_ab24	4	B4_N0	PN_F10	2.5 V (default)		8mA (default)	2 (default)		
f0	Output	PN_j22	6	B6_N0	PN_D15	2.5 V (default)		8mA (default)	2 (default)		
f1	Output	PN_l23	5	B5_N1	PN_C10	2.5 V (default)		8mA (default)	2 (default)		
f2	Output	PN_w27	5	B5_N1	PN_C7	2.5 V (default)		8mA (default)	2 (default)		
f3	Output	PN_af23	4	B4_N0	PN_G11	2.5 V (default)		8mA (default)	2 (default)		
g0	Output	PN_h22	6	B6_N0	PN_B17	2.5 V (default)		8mA (default)	2 (default)		
g1	Output	PN_h24	5	B5_N0	PN_J13	2.5 V (default)		8mA (default)	2 (default)		
g2	Output	PN_w26	5	B5_N1	PN_D6	2.5 V (default)		8mA (default)	2 (default)		
g3	Output	PN_y19	4	B4_N0	PN_C11	2.5 V (default)		8mA (default)	2 (default)		
output[2]	Output	PN_e25	7	B7_N1	PN_F12	2.5 V (default)		8mA (default)	2 (default)		
output[1]	Output	PN_e22	7	B7_N0	PN_J11	2.5 V (default)		8mA (default)	2 (default)		
output[0]	Output	PN_e21	7	B7_N0	PN_G14	2.5 V (default)		8mA (default)	2 (default)		
remainder[15]	Output	PN_g15	7	B7_N2	PN_A11	2.5 V (default)		8mA (default)	2 (default)		
remainder[14]	Output	PN_f15	7	B7_N2	PN_E14	2.5 V (default)		8mA (default)	2 (default)		
remainder[13]	Output	PN_h17	7	B7_N2	PN_B11	2.5 V (default)		8mA (default)	2 (default)		
remainder[12]	Output	PN_j16	7	B7_N2	PN_J15	2.5 V (default)		8mA (default)	2 (default)		
remainder[11]	Output	PN_h16	7	B7_N2	PN_D16	2.5 V (default)		8mA (default)	2 (default)		
remainder[10]	Output	PN_j15	7	B7_N2	PN_C12	2.5 V (default)		8mA (default)	2 (default)		
remainder[9]	Output	PN_g17	7	B7_N1	PN_D12	2.5 V (default)		8mA (default)	2 (default)		
remainder[8]	Output	PN_j17	7	B7_N2	PN_C14	2.5 V (default)		8mA (default)	2 (default)		
remainder[7]	Output	PN_h19	7	B7_N2	PN_E12	2.5 V (default)		8mA (default)	2 (default)		
remainder[6]	Output	PN_j19	7	B7_N2	PN_D9	2.5 V (default)		8mA (default)	2 (default)		
remainder[5]	Output	PN_e18	7	B7_N1	PN_B6	2.5 V (default)		8mA (default)	2 (default)		
remainder[4]	Output	PN_f18	7	B7_N1	PN_C9	2.5 V (default)		8mA (default)	2 (default)		
remainder[3]	Output	PN_e21	7	B7_N0	PN_B8	2.5 V (default)		8mA (default)	2 (default)		
remainder[2]	Output	PN_e19	7	B7_N0	PN_E10	2.5 V (default)		8mA (default)	2 (default)		
remainder[1]	Output	PN_f19	7	B7_N0	PN_A8	2.5 V (default)		8mA (default)	2 (default)		
remainder[0]	Output	PN_g19	7	B7_N2	PN_G9	2.5 V (default)		8mA (default)	2 (default)		

(4) 確認接線於正確腳位

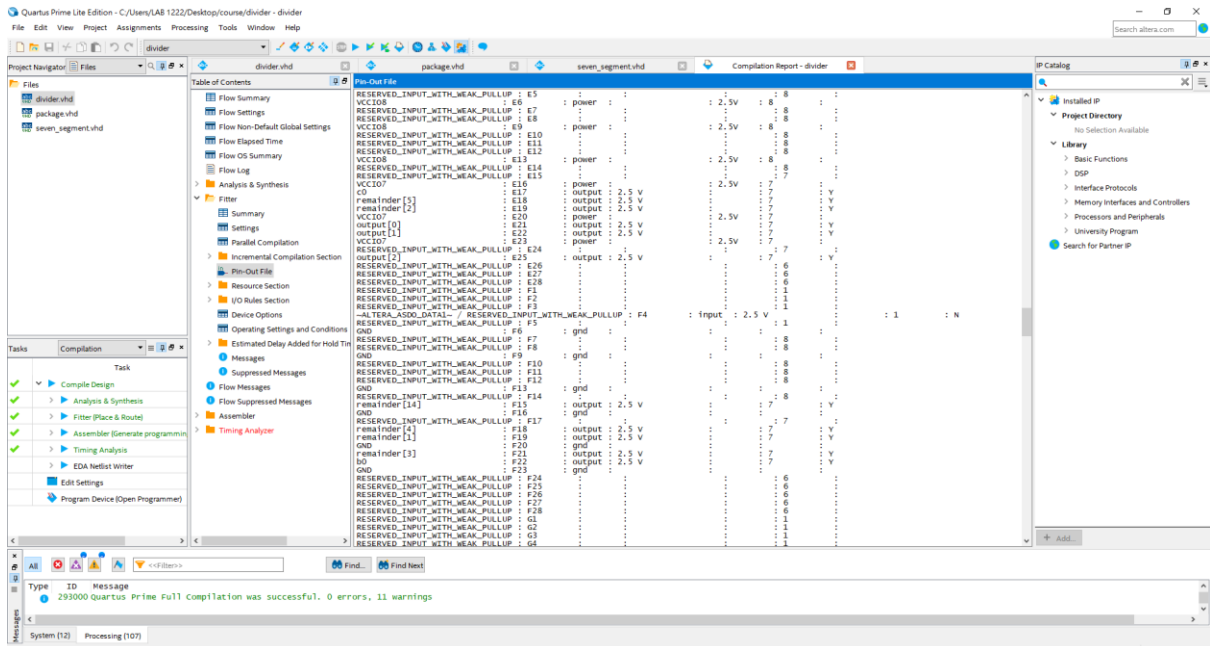


(5) 燒錄視窗設定及燒錄成功畫面

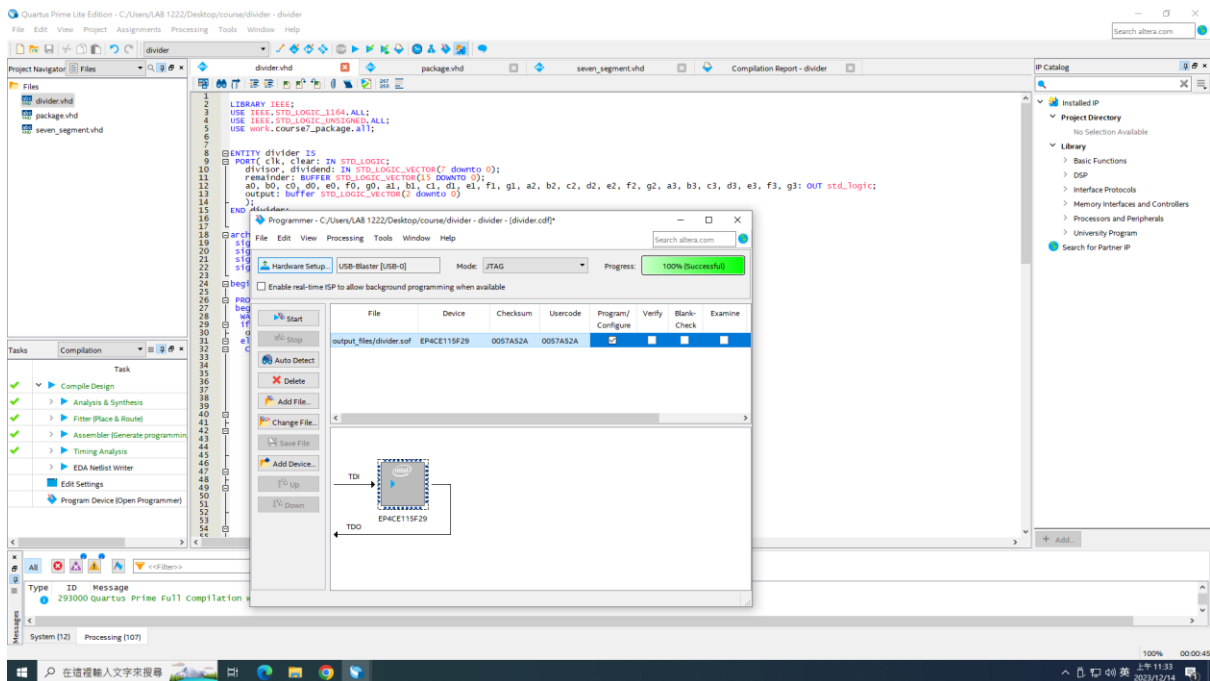

(五) 實驗結果


(1) 7 除以 2

輸出結果 Q: 3, R: 1

 

(2) 6 除以 2

Q: 3, R: 0

 

● 實際操作影片連結；

https://drive.google.com/file/d/1H41QsL72ab0y5Kg2CDLStdPW6-VORXHp/view?usp=drive_link

三、程式碼

divider.vhd

```
LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_UNSIGNED.ALL;

USE work.course7_package.all;

ENTITY divider IS

    PORT( clk, clear: IN STD_LOGIC;

        divisor, dividend: IN STD_LOGIC_VECTOR(7 downto 0);

        remainder: BUFFER STD_LOGIC_VECTOR(15 DOWNT0 0);

        a0, b0, c0, d0, e0, f0, g0, a1, b1, c1, d1, e1, f1, g1, a2, b2, c2, d2, e2, f2, g2, a3, b3, c3, d3, e3, f3, g3: OUT std_logic;

        output: buffer STD_LOGIC_VEcTOR(2 downto 0)

    );

END divider;
```

architecture main of divider is

signal w : STD_LOGIC := '0';

signal re : INTEGER := 0;

signal run : std_logic;

signal temp_s, temp_p: STD_LOGIC_VECTOR(15 downto 0);

begin

PROCESS

begin

WAIT UNTIL Clk'EVENT AND clk = '1';

if clear = '1' then

output <= "100";

else

Case output is

when "000" =>

output <= "111";


```
when "111" =>
```

```
    output <= "001";
```

```
when "001" =>
```

```
    if w = '1' then
```

```
        output <= "011";
```

```
    else
```

```
        output <= "010";
```

```
    end if;
```

```
when "011" =>
```

```
    if w = '1' then
```

```
        output <= "101";
```

```
    else
```

```
        output <= "001";
```

```
    end if;
```

```
when "010" =>
```

```
    if w = '1' then
```

```

output <= "101";

else

output <= "001";

end if;


when "100"=>

output <= "000";


when others =>

output <= "110";


end Case;

end if;

end PROCESS;


case3: temp_s <= (( remainder(15 downto 8) - divisor) & remainder(7 downto 0));

case4: temp_p <= (( remainder(15 downto 8) + divisor) & remainder(7 downto 0));


output_select: process

```



```
begin
```

```
WAIT UNTIL Clk'EVENT AND clk = '1';
```

```
case output is
```

```
when "000" =>
```

```
remainder <= ("00000000" & dividend);
```

```
when "111" =>
```

```
for_1: FOR i IN 14 downto 0 loop
```

```
    remainder(i + 1) <= remainder(i);
```

```
END loop;
```

```
remainder(0) <= '0';
```

```
when "001" =>
```

```
remainder <= (( remainder(15 downto 8) - divisor) & remainder(7 downto 0));
```

```
when "011" =>
```

```
for_2: FOR i IN 14 downto 0 loop
```

```
    remainder(i + 1) <= remainder(i);
```

```
END loop;
```

```
remainder(0) <= '1';
```

```
when "010" =>
```

```
for_3: FOR i IN 14 downto 0 loop
```

```
    remainder(i + 1) <= temp_p(i);
```

```
END loop;
```

```
remainder(0) <= '0';
```

```
when "100"=>
```

```
remainder <= "0000000000000000";
```

```
when "101" =>
```

```
for_r: FOR i IN 8 to 14 loop
```

```
    remainder(i) <= remainder(i + 1);
```

```
END loop;
```

```
remainder(15) <= '0';
```

```
remainder(7 downto 0) <= remainder(7 downto 0);
```

```
when others =>
```

```

    remainder <= remainder;

end Case;

end process;

count:process
begin

    WAIT UNTIL Clk'EVENT AND clk = '1';

    if clear = '1' then

        re <= 0;

    elsif output = "001" and run = '1' then

        re <= re + 1;

    else

        re <= re;

    end if;

end process;

run <= '0' when re = 8 else '1';

with output select

```

```

w <= not temp_s(15) when "001",

not run when "011",

not run when "010",

'0' when others;

show: seven_segment PORT MAP( remainder(11),remainder(10),remainder(9),remainder(8), re
mainder(15), remainder(14),remainder(13),remainder(12), remainder(3), remainder(2), remainder
(1),remainder(0), remainder(7), remainder(6),remainder(5),remainder(4),      a0, b0, c0, d0, e0, f
0, g0, a1, b1, c1, d1, e1, f1, g1, a2, b2, c2, d2, e2, f2, g2, a3, b3, c3, d3, e3, f3, g3);

end main;

```

package. vhd

```
LIBRARY ieee;

USE ieee.std_logic_1164.all;

PACKAGE course7_package IS

    component seven_segment

        PORT( W0, X0, Y0, Z0,

              W1, X1, Y1, Z1,

              W2, X2, Y2, Z2,

              W3, X3, Y3, Z3      : IN STD_LOGIC;

              a0, b0, c0, d0, e0, f0, g0,

              a1, b1, c1, d1, e1, f1, g1,

              a2, b2, c2, d2, e2, f2, g2,

              a3, b3, c3, d3, e3, f3, g3: OUT STD_LOGIC);

    END component seven_segment;

END course7_package;
```

seven_segment.vhd

```
Library ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY seven_segment IS
```

```
    PORT( W0, X0, Y0, Z0,
```

```
          W1, X1, Y1, Z1,
```

```
          W2, X2, Y2, Z2,
```

```
          W3, X3, Y3, Z3    : IN STD_LOGIC;
```

```
          a0, b0, c0, d0, e0, f0, g0,
```

```
          a1, b1, c1, d1, e1, f1, g1,
```

```
          a2, b2, c2, d2, e2, f2, g2,
```

```
          a3, b3, c3, d3, e3, f3, g3: OUT STD_LOGIC);
```

```
END seven_segment;
```

```
ARCHITECTURE LogicFunc OF seven_segment IS
```

```
BEGIN
```

```
    a0 <= (NOT W0 AND NOT X0 AND NOT Y0 AND Z0)
```

OR (NOT W0 AND X0 AND NOT Y0 AND NOT Z0)

OR (W0 AND NOT X0 AND Y0 AND Z0)

OR (W0 AND X0 AND NOT Y0);

b0 <= (NOT W0 AND X0 AND NOT Y0 AND Z0)

OR (NOT W0 AND X0 AND Y0 AND NOT Z0)

OR (W0 AND NOT X0 AND Y0 AND Z0)

OR (W0 AND X0 AND NOT Z0)

OR (W0 AND X0 AND Y0);

c0 <= (NOT W0 AND NOT X0 AND Y0 AND NOT Z0)

OR (W0 AND X0 AND NOT Z0)

OR (W0 AND X0 AND Y0);

d0 <= (NOT X0 AND NOT Y0 AND Z0)

OR (NOT W0 AND X0 AND NOT Y0 AND NOT Z0)

OR (X0 AND Y0 AND Z0)

OR (W0 AND NOT X0 AND Y0 AND NOT Z0);

e0 <= (NOT W0 AND Z0)

OR (NOT W0 AND X0 AND NOT Y0)

OR (NOT X0 AND NOT Y0 AND Z0);

f0 <= (NOT W0 AND NOT X0 AND Z0)

OR (NOT W0 AND NOT X0 AND Y0)

OR (NOT W0 AND Y0 AND Z0)

OR (W0 AND X0 AND NOT Y0);

$g_0 \leq (\text{NOT } W_0 \text{ AND NOT } X_0 \text{ AND NOT } Y_0)$

OR (NOT W0 AND X0 AND Y0 AND Z0);

$a_1 \leq (\text{NOT } W_1 \text{ AND NOT } X_1 \text{ AND NOT } Y_1 \text{ AND } Z_1)$

OR (NOT W1 AND X1 AND NOT Y1 AND NOT Z1)

OR (W1 AND NOT X1 AND Y1 AND Z1)

OR (W1 AND X1 AND NOT Y1);

$b_1 \leq (\text{NOT } W_1 \text{ AND } X_1 \text{ AND NOT } Y_1 \text{ AND } Z_1)$

OR (NOT W1 AND X1 AND Y1 AND NOT Z1)

OR (W1 AND NOT X1 AND Y1 AND Z1)

OR (W1 AND X1 AND NOT Z1)

OR (W1 AND X1 AND Y1);

$c_1 \leq (\text{NOT } W_1 \text{ AND NOT } X_1 \text{ AND } Y_1 \text{ AND NOT } Z_1)$

OR (W1 AND X1 AND NOT Z1)

OR (W1 AND X1 AND Y1);

$d_1 \leq (\text{NOT } X_1 \text{ AND NOT } Y_1 \text{ AND } Z_1)$

OR (NOT W1 AND X1 AND NOT Y1 AND NOT Z1)

OR (X1 AND Y1 AND Z1)

OR (W1 AND NOT X1 AND Y1 AND NOT Z1);

e1 <= (NOT W1 AND Z1)

OR (NOT W1 AND X1 AND NOT Y1)

OR (NOT X1 AND NOT Y1 AND Z1);

f1 <= (NOT W1 AND NOT X1 AND Z1)

OR (NOT W1 AND NOT X1 AND Y1)

OR (NOT W1 AND Y1 AND Z1)

OR (W1 AND X1 AND NOT Y1);

g1 <= (NOT W1 AND NOT X1 AND NOT Y1)

OR (NOT W1 AND X1 AND Y1 AND Z1);

a2 <= (NOT W2 AND NOT X2 AND NOT Y2 AND Z2)

OR (NOT W2 AND X2 AND NOT Y2 AND NOT Z2)

OR (W2 AND NOT X2 AND Y2 AND Z2)

OR (W2 AND X2 AND NOT Y2);

b2 <= (NOT W2 AND X2 AND NOT Y2 AND Z2)

OR (NOT W2 AND X2 AND Y2 AND NOT Z2)

OR (W2 AND NOT X2 AND Y2 AND Z2)

OR (W2 AND X2 AND NOT Z2)

OR (W2 AND X2 AND Y2);

c2 <= (NOT W2 AND NOT X2 AND Y2 AND NOT Z2)

OR (W2 AND X2 AND NOT Z2)

OR (W2 AND X2 AND Y2);

d2 <= (NOT X2 AND NOT Y2 AND Z2)

OR (NOT W2 AND X2 AND NOT Y2 AND NOT Z2)

OR (X2 AND Y2 AND Z2)

OR (W2 AND NOT X2 AND Y2 AND NOT Z2);

e2 <= (NOT W2 AND Z2)

OR (NOT W2 AND X2 AND NOT Y2)

OR (NOT X2 AND NOT Y2 AND Z2);

f2 <= (NOT W2 AND NOT X2 AND Z2)

OR (NOT W2 AND NOT X2 AND Y2)

OR (NOT W2 AND Y2 AND Z2)

OR (W2 AND X2 AND NOT Y2);

g2 <= (NOT W2 AND NOT X2 AND NOT Y2)

OR (NOT W2 AND X2 AND Y2 AND Z2);

$a_3 \leq (\text{NOT } W_3 \text{ AND NOT } X_3 \text{ AND NOT } Y_3 \text{ AND } Z_3)$

$\text{OR } (\text{NOT } W_3 \text{ AND } X_3 \text{ AND NOT } Y_3 \text{ AND NOT } Z_3)$

$\text{OR } (W_3 \text{ AND NOT } X_3 \text{ AND } Y_3 \text{ AND } Z_3)$

$\text{OR } (W_3 \text{ AND } X_3 \text{ AND NOT } Y_3);$

$b_3 \leq (\text{NOT } W_2 \text{ AND } X_2 \text{ AND NOT } Y_3 \text{ AND } Z_3)$

$\text{OR } (\text{NOT } W_3 \text{ AND } X_3 \text{ AND } Y_3 \text{ AND NOT } Z_3)$

$\text{OR } (W_3 \text{ AND NOT } X_3 \text{ AND } Y_3 \text{ AND } Z_3)$

$\text{OR } (W_3 \text{ AND } X_3 \text{ AND NOT } Z_3)$

$\text{OR } (W_3 \text{ AND } X_3 \text{ AND } Y_3);$

$c_3 \leq (\text{NOT } W_3 \text{ AND NOT } X_3 \text{ AND } Y_3 \text{ AND NOT } Z_3)$

$\text{OR } (W_3 \text{ AND } X_3 \text{ AND NOT } Z_3)$

$\text{OR } (W_3 \text{ AND } X_3 \text{ AND } Y_3);$

$d_3 \leq (\text{NOT } X_3 \text{ AND NOT } Y_3 \text{ AND } Z_3)$

$\text{OR } (\text{NOT } W_3 \text{ AND } X_3 \text{ AND NOT } Y_3 \text{ AND NOT } Z_3)$

$\text{OR } (X_3 \text{ AND } Y_3 \text{ AND } Z_3)$

$\text{OR } (W_3 \text{ AND NOT } X_3 \text{ AND } Y_3 \text{ AND NOT } Z_3);$

$e_3 \leq (\text{NOT } W_3 \text{ AND } Z_3)$

$\text{OR } (\text{NOT } W_3 \text{ AND } X_3 \text{ AND NOT } Y_3)$

```
OR (NOT X3 AND NOT Y3 AND Z3);

f3 <= (NOT W3 AND NOT X3 AND Z3)

OR (NOT W3 AND NOT X3 AND Y3)

OR (NOT W3 AND Y3 AND Z3)

OR (W3 AND X3 AND NOT Y3);

g3 <= (NOT W3 AND NOT X3 AND NOT Y3)

OR (NOT W3 AND X3 AND Y3 AND Z3);

END LogicFunc;
```